

Third Semester B.E. Makeup Examination, January 2020
DIGITAL ELECTRONICS

Time: 3 Hours

Max. Marks: 100

Instructions: 1. Answer any one question from each Unit.

UNIT - I

L CO PO M

- 1 a. Solve the following Boolean Expression to get the reduced form and draw the logic circuit using NAND gates only. $Y = B + AB' + ACD + AC'$
 (3) (1) (1) (06)
- b. Apply K-Map reduction technique to obtain the reduced POS expression for the given Boolean function.
 $F(A,B,C,D) = \prod M(0,1,5,9,13,14,15) + d(3,4,7,10,11)$
 (3) (1) (2) (06)
- c. Solve the given Boolean function by using Quine Mc Clusky method and find the essential prime implicants.
 $F(A,B,C,D) = \sum m(1,3,5,10,11,12,13,14,15)$
 (3) (1) (2) (08)

OR

- 2 a. Realize the given Boolean expression using NAND gates and find the minterms for the same.
 $F = AC + AB'C + ACD$
 (2) (1) (1) (06)
- b. Make use of K-Map reduction technique to obtain the reduced SOP expression for the given Boolean function.
 $F(A,B,C,D) = \sum m(0,1,5,9,13,14,15) + d(3,4,7,10,11)$
 (3) (1) (2) (06)
- c. Identify all the prime and essential prime implicants of the following Boolean function using Quine Mc Clusky method.
 $F(A,B,C,D) = \sum m(2,3,6,7,8,9,13,15)$
 (3) (1) (2) (08)

UNIT - II

- 3 a. Define a Multiplexer. Implement the given Boolean function using 8:1 multiplexer. Consider D as MEV.
 $F(A,B,C,D) = \sum m(0,1,3,4,5,7,9,11,13,15)$
 (3) (2) (1) (06)
- b. Design and illustrate a 1-bit magnitude comparator with a neat diagram and truth table.
 (3) (2) (2) (06)
- c. Define Decoder. Design and explain a BCD-to-Decimal decoder.
 (3) (2) (2) (08)

OR

- 4 a. Design a 4-bit odd parity generator. Write any one application of the same.
 (2) (2) (1) (06)
- b. Compare Decoder and Demultiplexer., make use of suitable Decoder and multi-input OR gate to implement the following functions.
 $F1(A,B,C) = \sum m(1,3,7)$ $F2(A,B,C) = \sum m(2,3,5)$ $F3 = \sum m(0,1,5,7)$
 (2) (2) (2) (06)
- c. How a PAL is different from PLA? Realize the following functions using PAL.
 $Y1 = A'B'C' + A'BC + A'BC' + ABC'$
 $Y2 = ABC$
 (1) (2) (2) (08)

Note: L (Level), CO (Course Outcome), PO (Programme Outcome), M (Marks)

UNIT - III

- 5 a. Explain propagation delay time. If propagation delay is 20 nano seconds what is the maximum clock frequency. Draw the circuit for PT forming circuit. (3) (3) (1) (06)
- b. Realize SR flip flop using NOR gates. (3) (3) (2) (06)
- c. Derive the characteristics equations for SR, JK flip flops with state transition diagram and write the excitation tables. (3) (3) (2) (08)

OR

- 6 a. Explain working of (i) gated JK flip flop (ii) gated D flip flop. (2) (3) (1) (06)
- b. Explain working of JK master slave flip flop. (2) (3) (1) (06)
- c. Derive the characteristics equations for T, JK flip flops with state transition diagram and write the excitation tables (3) (3) (2) (08)

UNIT - IV

- 7 a. List out the applications of a shift register and with a neat logic diagram explain the working of serial adder. (2) (3) (1) (06)
- b. How to convert JK flip flop into T flip flop and explain the steps. (1) (3) (1) (06)
- c. Design a MOD-6 synchronous upcounter using JK flip flops and explain its operation with a neat logic diagram and truth table. (3) (3) (2) (08)

OR

- 8 a. Develop the logic diagram of a 4 bit Serial In Parallel Out shift register and explain its working. (3) (3) (2) (06)
- b. Explain with a neat diagram and Truth Table 3-bit Ripple down counter using JK flip flops. (2) (3) (1) (06)
- c. Design a MOD-8 synchronous upcounter using JK flip flops and explain its operation with a neat logic diagram and truth table. (3) (3) (1) (08)

UNIT - V

- 9 a. Explain the working of 2-bit Simultaneous A/D converter. (2) (3) (1) (06)
- b. Develop verilog program for following circuits in Data flow model.
1. 4:1 Multiplexer 2. 1-bit Full Adder (3) (4) (2) (06)
- c. Explain 4-bit R-2R ladder Digital to Analog converter and find the output for the input 1001 and 1100 when $V = +5$ volts. (2) (3) (1) (08)

OR

- 10 a. Explain the working of 4-bit Successive Approximation type A/D converter. (2) (3) (1) (06)
- b. Develop verilog program for following circuits in Data flow model.
1. 2:4 Decoder 2. 8:1 Multiplexer (3) (4) (2) (06)
- c. Explain 4-bit R-2R ladder DAC and find the output when DAC input is 11010 and voltage $v = +5$ V. Also what is the voltage resolution? (2) (3) (1) (08)

Note: L (Level), CO (Course Outcome), PO (Programme Outcome), M (Marks)

Third Semester B.E. Semester End Examination, Dec./Jan. 2019-20
DIGITAL ELECTRONICS

Time: 3 Hours

Max. Marks: 100

Instructions: I. Answer one full question from each unit.


UNIT - I

L CO PO M

- 1 a. Solve the given Boolean function using Boolean algebra and realize using NAND gates.
 $Y = A'BC + ABC + ABC' + AB$
 (3) (1) (1) (06)
- b. Make use of K-Map reduction technique to obtain the simplified SOP expression for the given Boolean function and realize using logic gates.
 $F(A,B,C,D) = \sum m(2,3,4,5,6,7,10,11,12)$
 (3) (1) (2) (06)
- c. Apply Quine McClusky reduction technique to simplify the given Boolean expression and draw the logic circuit for the same.
 $F(A,B,C,D) = \sum m(0,1,2,3,4,5,12,13,14) + d(6,15)$
 (3) (1) (2) (08)

OR

 - 2 a. List the minterms for the given logic circuit.



- (3) (1) (1) (06)
- b. Make use of K-Map reduction technique to obtain the simplified POS expression for the given Boolean function and realize by using NOR gates.
 $F(A,B,C,D) = \prod M(0,1,4,5,8,12,13)$
 (3) (1) (2) (06)
- c. Apply Quine McClusky reduction technique to simplify the given Boolean expression and find essential prime implicants.
 $F(A,B,C,D) = \sum m(1,3,5,7,12,13,14,15)$
 (3) (1) (2) (08)

UNIT - II

L CO PO M

- 3 a. Implement the given Boolean function using 8:1 multiplexer. Consider A as MEV.
 $F(A,B,C,D) = \sum m(0,1,3,4,5,7,9,11,13,15)$
 (3) (2) (2) (06)
- b. Define decoder. Implement following functions using suitable decoder
 $f_1(A,B,C) = \sum m(0,1,6)$
 $f_2(A,B,C) = \sum m(2,4,6)$
 (3) (2) (1) (06)
- c. Design 2-bit magnitude comparator with the help of neat logic diagram. Implement the same using basic gates.
 (3) (2) (2) (08)

Note: L (Level), CO (Course Outcome), PO (Programme Outcome), M (Marks)

OR

- 4 a. Design an Odd parity generator circuit for 3-bit binary data. (3) (2) (2) (06)
- b. Define Multiplexer. Explain the working of 4:1 multiplexer. Implement the given Boolean function using 4:1 multiplexer using A as MEV.
 $F(A,B,C) = \sum m(0,2,4,7)$ (3) (2) (2) (06)
- c. Differentiate between PAL and PLA. Implement the following Boolean functions using PLA.
 $f_1(A,B,C) = \sum m(0,1,7)$
 $f_2(A,B,C) = \sum m(4,5,7)$ (3) (2) (2) (08)

UNIT - III

L CO PO M

- 5 a. Illustrate the working of a positive edge triggered SR flip flop and draw a neat sketch of its output waveforms. (2) (3) (1) (06)
- b. Determine the characteristic equations of SR, T and D flip flops. (5) (3) (2) (06)
- c. With a neat circuit diagram explain the working of a master-slave JK flip flop and write the advantages. (2) (3) (1) (06)

OR

- 6 a. Compare a latch and a flip flop? Construct SR latch using NAND/NOR gates. (2) (3) (1) (06)
- b. Explain the characteristics of an ideal clock and find the clock frequency for a system when the cycle time is 5ns. (2) (3) (1) (06)
- c. Derive the characteristic equations for SR, JK flip flops with state transition diagram and write the excitation tables. (2) (3) (1) (08)

UNIT - IV

L CO PO M

- 7 a. Show how SR flip flop is converted to JK flip flop. (3) (3) (2) (06)
- b. Explain with neat waveform 4 bit Johnson counter. (2) (3) (2) (06)
- c. Design MOD-6 synchronous counter using JK flip flop. Draw the logic diagram for the same. (4) (3) (2) (08)
- 8 a. Show how JK flip flop is converted into T flip flop. (3) (3) (2) (06)
- b. Explain with neat waveform 4 bit ring counter. (2) (3) (2) (06)
- c. Analyze the given sequential circuit and draw state diagram for same.



(4) (3) (2) (08)

Note: L (Level), CO (Course Outcome), PO (Programme Outcome), M (Marks)

UNIT -V

- | | | L | CO | PO | M |
|---|--------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|-----|-----|------|
| 9 | a. Explain the working of 2 bit parallel comparator(simultaneous conversion) A/D Converter with neat circuit diagram. | (2) | (3) | (2) | (06) |
| | b. Write HDL program for 4:1 multiplexer and full adder. | (3) | (4) | (2) | (06) |
| | c. With neat sketch explain the working of 4 bit R-2R binary ladder DAC. Define resolution of D/A converter. What is resolution for 8 bit DAC if $V = +5V$. | (2) | (3) | (1) | (08) |

OR

- | | | | | | |
|----|--------------------------------------------------------------------------------------------------------------------------------|-----|-----|-----|------|
| 10 | a. Explain the working of 4 bit successive approximation ADC with neat circuit diagram. | (2) | (3) | (1) | (06) |
| | b. Explain the working of R-2R ladder DAC. Find the output voltages for the inputs 11000 and 10010 if Logic 0= 0V and 1 =+10V. | (2) | (3) | (1) | (08) |
| | c. Write HDL program for (i) $Y = ABC + AB'C + AB$ (ii) 2:4 decode | (3) | (4) | (2) | (06) |